


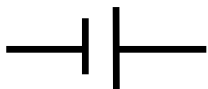

Name: _____

Date: _____

ESL Kids World: Parallel and Series Circuits

Draw the circuits. Use the circuit symbols.

Circuit Symbols

Switch	
Energy Source	
Resistor	

Draw a parallel circuit

Draw a series circuit



Copyright © 2020 www.eslkidsworld.com

